Ohm's Law

| | liscovered the mathematical relationship between:(),() |
|--------------------------------|--|
| Formula: | OR |
| | alculations, you must are required for full marks. 1. Write down the you require. 2 in the known values. 3. Write down your with |
| | ations: Show your work. 3 steps for each answer!!! as a 3V battery and a current of 2A, what is the resistance? |
| 2. What is the v | oltage through a 10 🕰 light bulb that has 2A flowing through it? |
| 3. If a 6V batter the circuit? | ry is used with a 15 1. bulb, what is the current flowing through |