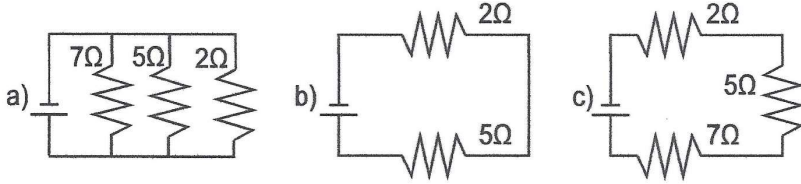


Name: \_\_\_\_\_


Blk: \_\_\_\_\_ Date: \_\_\_\_\_

**Science 9**  
**TYPES OF CIRCUITS WORKSHEET**

1. Determine the **total resistance** for each of the following circuits below.




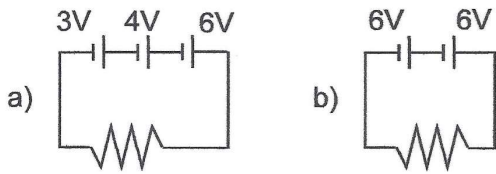2. Determine the **total voltage** (electric potential) for each of the following circuits below.




3. Fill out the table for the circuit diagramed at the right. (Use **pHet** to get Voltage Values & Calculate Current)

Circuit Position	Voltage (V)	Current (A)	Resistance ( $\Omega$ )
1			10.0 $\Omega$
2			20.0 $\Omega$
3			30.0 $\Omega$
Total	6.00 V		

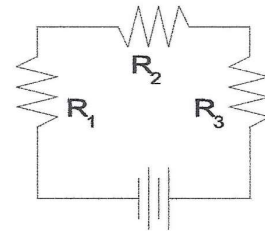


4. Fill out the table for the circuit diagramed at the right. (Use **pHet** to get Voltage Values & Calculate Current)

Circuit Position	Voltage (V)	Current (A)	Resistance ( $\Omega$ )
1			10.0 $\Omega$
2			20.0 $\Omega$
3			30.0 $\Omega$
Total	6.00 V		

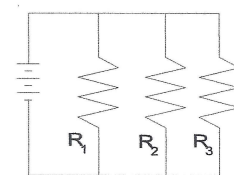


5. Fill out the table for the circuit diagramed at the right. (Use **pHet** to get Voltage Values & Calculate Current)

Circuit Position	Voltage (V)	Current (A)	Resistance ( $\Omega$ )
1			10.0 $\Omega$
2			20.0 $\Omega$
3			30.0 $\Omega$
Total	6.00 V		

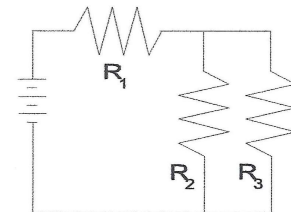

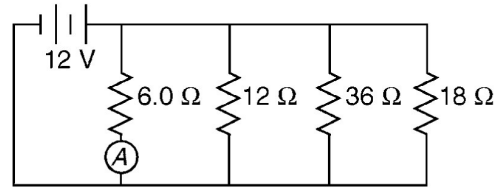**Questions 6 and 7** refer to the following:

The diagram below represents an electric circuit consisting of four resistors and a 12-volt battery




6) Calculate the **current** measured by ammeter *A* shown in the diagram?

7) What is the **total resistance** of the circuit shown?

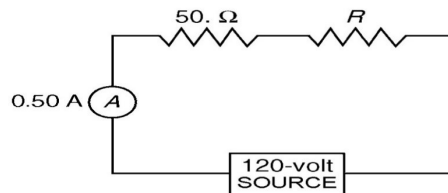**Questions 8 and 9** refer to the following:

A 50.-ohm resistor, an unknown resistor *R*, a 120-volt source, and an ammeter are connected in a complete circuit. The ammeter reads 0.50 ampere.



8) Calculate the:


a. **Voltage** of the 50- ohm resistor

b. **voltage of R** of the circuit shown.

9) **Determine the resistance** of resistor *R* shown in the diagram.

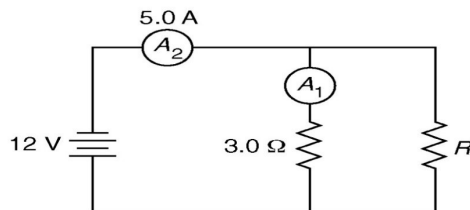**Questions 10 through 12** refer to the following:

A 3.0-ohm resistor, an unknown resistor, *R*, and two ammeters, *A*<sub>1</sub> and *A*<sub>2</sub>, are connected as shown below with a 12-volt source. Ammeter *A*<sub>2</sub> reads a current of 5.0 amperes.



10) Calculate the **resistance** of the unknown resistor, *R* in the diagram shown.

11) Calculate the **current** measured by ammeter *A*<sub>1</sub> in the diagram shown.

12) Determine the **total resistance** of the circuit shown.